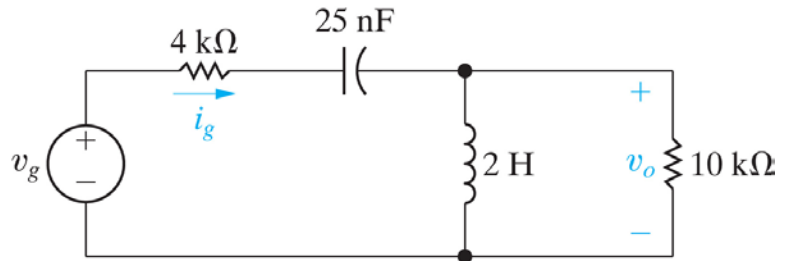


**Problem 1:**

In the circuit to the right, find the steady-state expression for  $v_o(t)$  if

$$v_g(t) = 45 \cos(10,000t) \text{ V.}$$

Hint: Use a voltage divider.





**Problem 2:**

A node with three branches is shown below. Suppose that this node is part of a circuit that is operating in the sinusoidal steady-state with

$$i_1(t) = 3 \cos(2000t - 45^\circ) \text{ mA} \quad i_2(t) = 4 \cos(2000t + 30^\circ) \text{ mA}$$

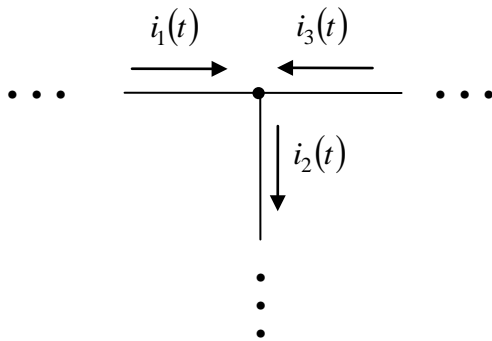What is the expression for the steady-state current  $i_3(t)$  in terms of a single cosine function?



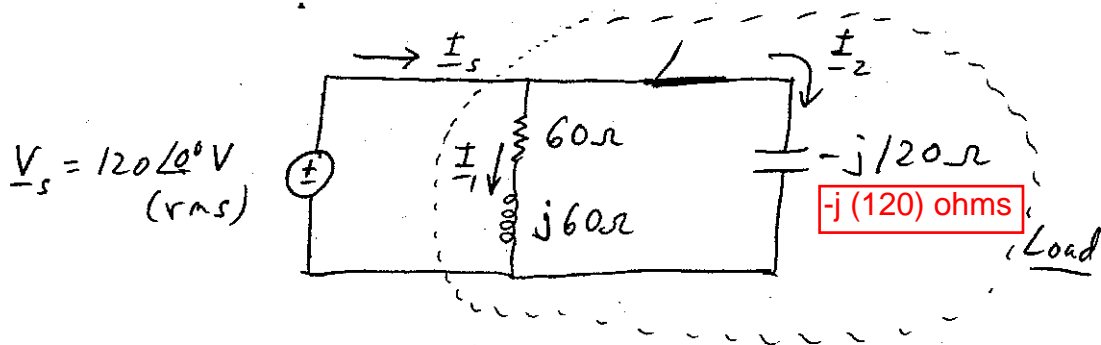

(a) For the branch containing the 60 ohm resistor and  $j60$  ohm inductor, please compute the following quantities and place your answers on the lines (including proper units).

Complex power \_\_\_\_\_

Average power \_\_\_\_\_

Apparent power \_\_\_\_\_

Peak amplitude of the current,  $i_1(t)$  \_\_\_\_\_

Power factor (include lagging/leading) \_\_\_\_\_

Maximum value of instantaneous power. \_\_\_\_\_

(b) For the *voltage source*, please compute the following quantities and place your answers on the lines (including proper units). The capacitor is connected in parallel with the resistor and inductor.

Complex power

---

Average power

---

Apparent power

---

Peak amplitude of the source current,  $i_s(t)$

---

Power factor (include lagging/leading)

---

Maximum value of instantaneous power.

---