
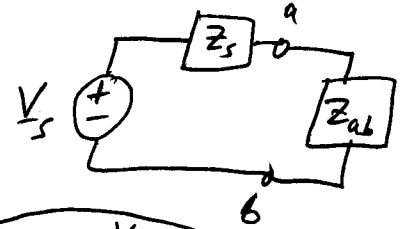


Linear Transformer Analysis

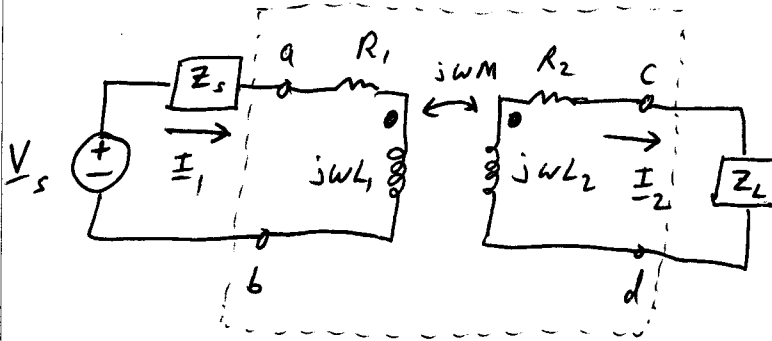

$$Z_{ab} = \frac{V_s}{I_1} - Z_s$$

$$V_s = (Z_s + R_1 + j\omega L_1) I_1 - j\omega M I_2 = Z_{11} I_1 - j\omega M I_2$$

$$0 = -j\omega M I_1 + (R_2 + j\omega L_2 + Z_L) I_2 = -j\omega M I_1 + Z_{22} I_2$$

$$I_1 = \frac{\begin{vmatrix} V_s & -j\omega M \\ 0 & Z_{22} \end{vmatrix}}{\begin{vmatrix} Z_{11} & -j\omega M \\ -j\omega M & Z_{22} \end{vmatrix}} = \frac{Z_{22} V_s}{Z_{11} Z_{22} + (\omega M)^2}$$

$$I_2 = \frac{\begin{vmatrix} Z_{11} & V_s \\ -j\omega M & 0 \end{vmatrix}}{\begin{vmatrix} Z_{11} & -j\omega M \\ -j\omega M & Z_{22} \end{vmatrix}} = \frac{j\omega M V_s}{Z_{11} Z_{22} + (\omega M)^2} = \frac{j\omega M}{Z_{22}} I_1$$

IDEAL TRANSFORMER

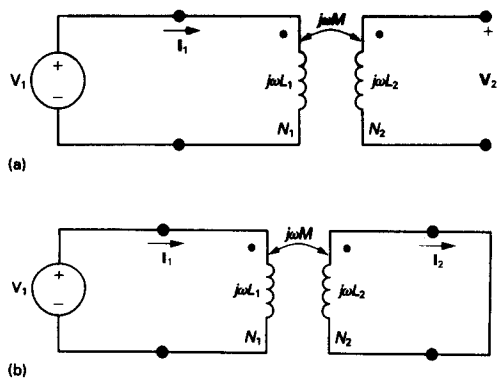


Figure 9.41 The circuits used to verify the volts-per-turn and ampere-turn relationships for an ideal transformer.

Assume:

- 1) $k = 1$
- 2) $L_1 = L_2 = \infty$
- 3) $R_1 = R_2 = 0$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \quad (9.83)$$

$$I_1 N_1 = I_2 N_2 \quad (9.86)$$

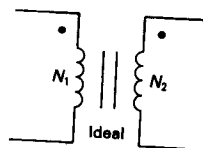


Figure 9.42 The graphic symbol for an ideal transformer.

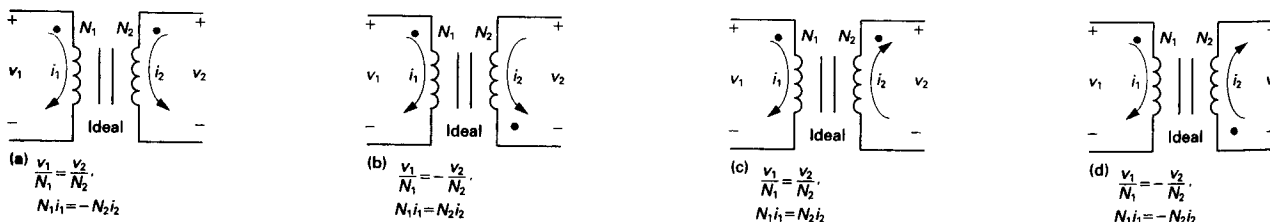


Figure 9.43 Circuits that show the proper algebraic signs for relating the terminal voltages and currents of an ideal transformer.

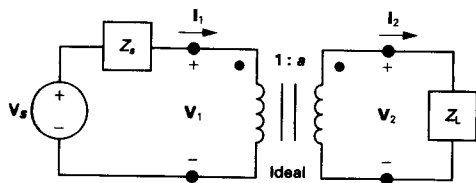


Figure 9.47 Using an ideal transformer to couple a load to a source.

$$Z_{IN} = \frac{V_1}{I_1}$$