
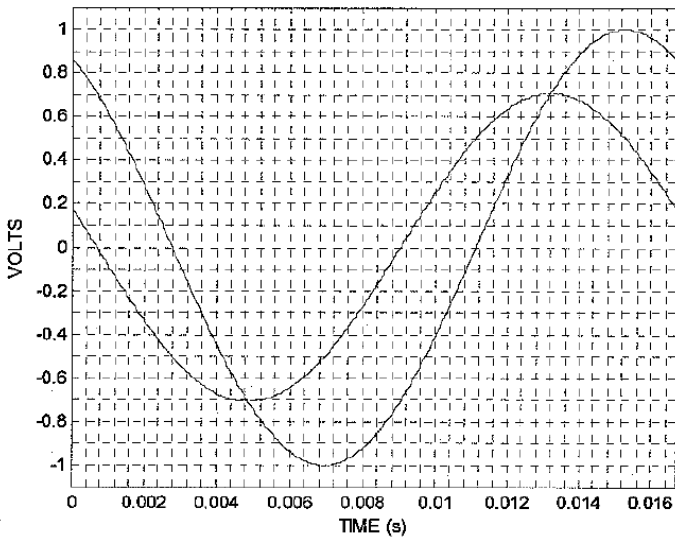
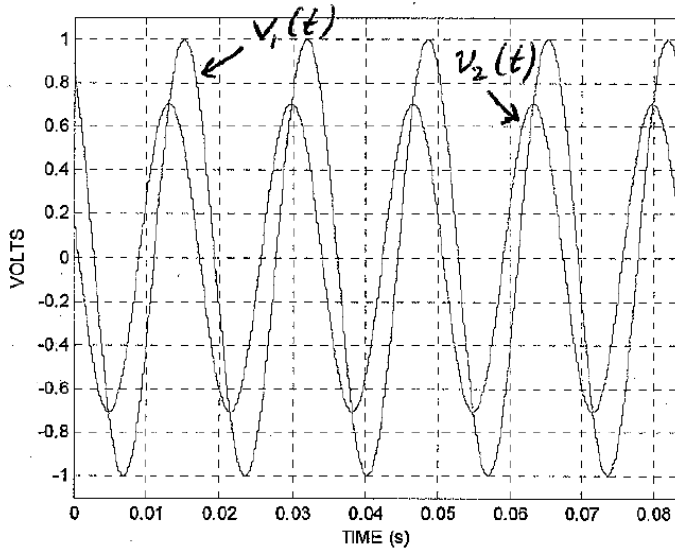


ELEC 226, Homework 2 Problem:

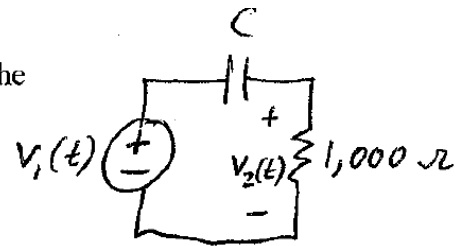The voltage waveforms for $v_1(t)$ and $v_2(t)$ in the circuit to the right are shown below in sinusoidal steady-state. Please estimate the value of the capacitance, C .



Expanded view of one cycle.