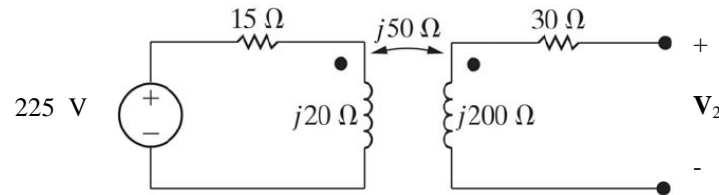


Homework 8: Supplemental Problem

Please answer the following for the sinusoidal steady-state circuit shown below

- (a) Find the voltage phasor \mathbf{V}_2 in the *linear* transformer circuit and express it in polar form (magnitude and angle).



- (b) Replace the linear transformer by an *ideal* transformer with turns ratio $1:a$ where

$$a = \sqrt{\frac{\omega L_2}{\omega L_1}} = \sqrt{\frac{200}{20}} = \sqrt{10}. \text{ Repeat part (a) and find the voltage phasor } \mathbf{V}_2.$$

Compare your answers. What is the value of $k = \frac{M}{\sqrt{L_1 L_2}}$? How accurate is the ideal transformer model for the circuit in part (a) with open-circuit load?