

PHYS 235

(A)

In-class exercise, Tuesday 1/22/19

I. Design a circuit to light a CEC 1432 miniature lamp as intended by the manufacturer.
Use D-cells (1.5 V) & resistors.

From the spec sheet we want

$$I_{\text{bulb}} = 0.160 \text{ A}$$


$$P = 0.512 \text{ W}$$

$$[\Delta V_{\text{bulb}} = 3.2 \text{ V}] \leftarrow \text{blocked out}$$

Can determine ΔV from power & current:

$$\begin{aligned} P &= I \Delta V \rightarrow \Delta V = \frac{P}{I} \\ &= \frac{0.512}{0.16} \\ &= 3.2 \text{ V} \end{aligned}$$

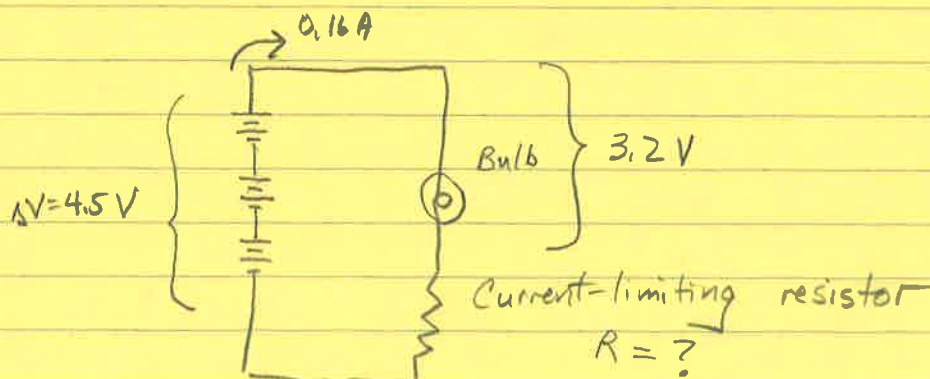Thus we need at least 3-D cells in series to get a potential difference greater than 3.2 V.



If we choose the right current limiting resistor to get $I = 0.16 \text{ A}$, the voltage drop across the resistor will be

$$\Delta V_R = 4.5 - 3.2 = 1.3 \text{ V}$$

We can get the value of the resistance from Ohm's Law:

$$R = \frac{\Delta V_R}{I} = \frac{1.3}{0.16} = 8.125 \Omega$$

8Ω will be "close enough."

II How long will the bulb stay lit under these conditions?

The Wikipedia page for "D Battery" gives a typical "capacity" for a Zinc-carbon D-cell as $8000 \text{ mA}\cdot\text{h}$ or equivalently $12 \text{ W}\cdot\text{h}$

$$\begin{aligned} \rightarrow t &= \frac{8000 \text{ mA}\cdot\text{h}}{0.16 \text{ A}} \\ &= 50 \text{ h} \end{aligned}$$


$$\begin{aligned} \rightarrow t &= \frac{12 \text{ W}\cdot\text{h}}{1.5 \text{ V} \times 0.16 \text{ A}} \\ &= 50 \text{ h} \end{aligned}$$

(This is shorter than the listed lifetime of the bulb; $\sim 3,000 \text{ h}$.)

★ Note: Some of power from the battery is dissipated in the resistor.

III Lighting two bulbs in series.

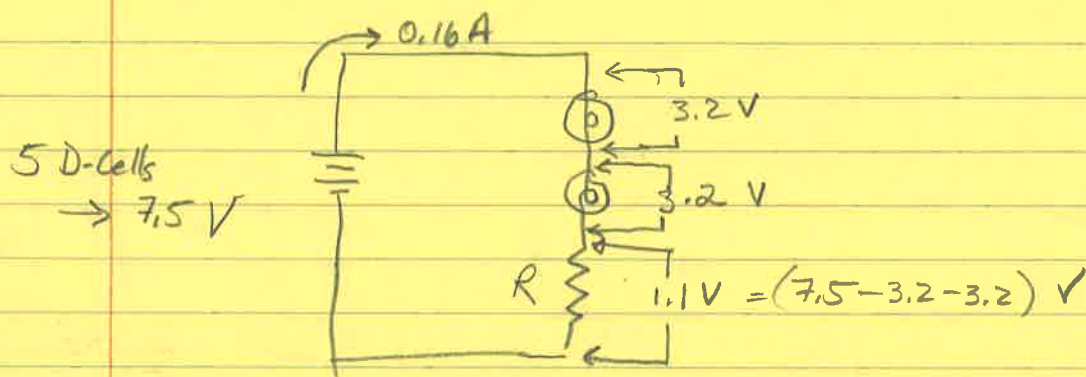For this we need a voltage difference greater than $2 \times 3.2V$. We can get this from 5 D-cells in series.




In this case $R = \frac{1.1V}{0.16A} \approx 7\Omega$

Each of batteries still has 0.16A flowing through it, so the lifetime is the same 50 h as before.

IV Lighting two bulbs in parallel

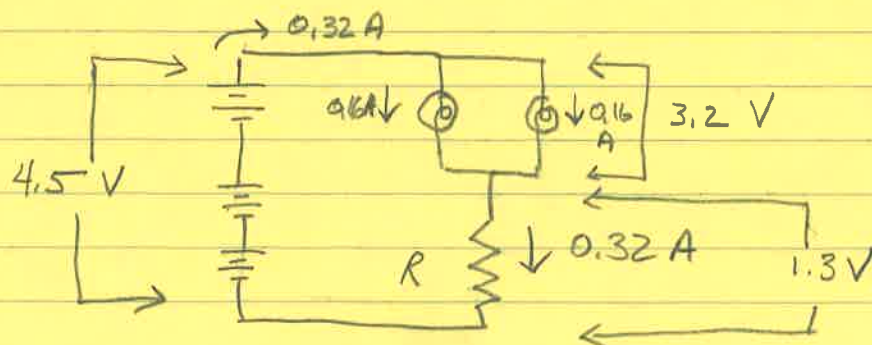We can simply add an additional bulb to the circuit from part I.




In this circuit

$$R = \frac{\Delta V}{I} = \frac{1.3V}{0.32A}$$
$$\approx 4\Omega$$

The current through each battery is twice as big as in I , so the battery lifetime will be cut in half $\rightarrow 25h$.

B In-class exercise, Tuesday 1/22/19

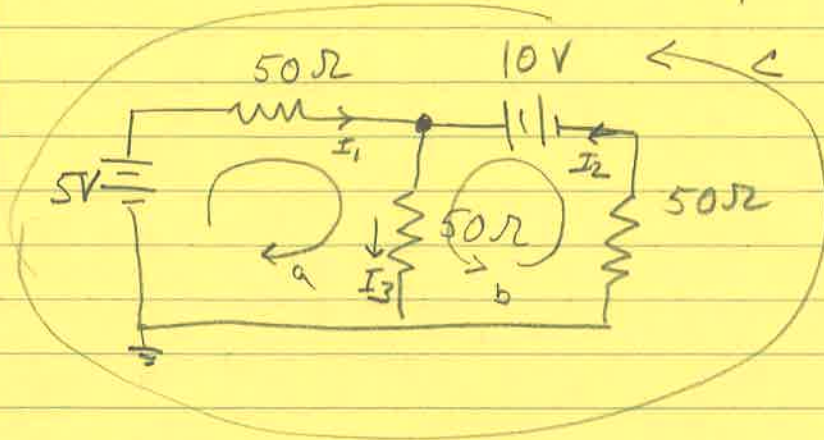

KCL at top node:

$$I_1 + I_2 = I_3$$

KVL:

Loop a: $5 - 50I_1 - 50I_3 = 0$

Loop b: $10 - 50I_3 - 50I_2 = 0$

Loop c: $10 + 50I_1 - 5 - 50I_2 = 0$

} Only need 2 of these equations.

One way to solve:

Add "loop a" equation to "loop b" equation

$$\rightarrow 15 - 50(I_1 + I_2) - 100I_3 = 0$$

Use KCL

$$15 - 50I_3 - 100I_3 = 0$$

$$\rightarrow I_3 = \frac{15}{150} = 0.100 \text{ A} = 100 \text{ mA}$$

Use "Loop a" equation

$$\cancel{5} - 50I_1 - \cancel{50 \times 0.1} = 0$$

$$50 I_1 = 0$$

$$\Rightarrow I_1 = 0$$

$$\Rightarrow I_2 = 0.1 \text{ A} = 100 \text{ mA}$$