## Topic 4

# RC Circuits: Response to Step Functions — the *Time Domain*

Material discussed 1/29/19

#### 4.1 Capacitors



- Capacitors are physical breaks in circuits.
- Capactors store an amount of charge that is proportional to the potential difference across the capacitor:

$$Q_C = C \Delta V_C$$
 or  $C = \frac{Q_C}{\Delta V_C}$ 

- SI unit of capacitance is Farads (F).
- Capacitors block DC current; pass (in a sense) AC current.
- •

$$I = \frac{dQ_C}{dt}$$
$$\rightarrow C \frac{dV_C}{dt}$$



Figure 4.1: Simple *RC* cicuit.

• Capacitors in parallel:

$$C_{\rm eq} = C_1 + C_2.$$

• Capacitors in series:

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$$
 or  $C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$ .

### 4.2 Charging and discharging in *RC* circuits (qualitative)

• Charging of a capacitor through a resistor:



• Discharging of a capacitor through a resistor:



#### 4.3 Differential Equations

- The solution of a differential equation is a function.
- Functional solutions of differential equations have undetermined constants.
- Undetermined constants can be fixed by considering *initial conditions*.

### 4.4 Charging and discharging in *RC* circuits (quantitative)

- Derivations: Kirchoff's voltage law (loop rule)  $\rightarrow$  differential equation.
- Discharging of a capacitor through a resistor Kirchoff's voltage law (loop rule):

$$V_C - IR = 0 \longrightarrow V_C + RC \frac{dV_C}{dt} = 0 \longrightarrow \frac{dV_C}{dt} = -\frac{1}{RC} V_C$$

Initial Condition:

$$V_C(0) = V_0 = \frac{Q_0}{C}$$

Solution:

$$V_C(t) = V_0 e^{-t/RC} \longrightarrow Q_C(t) = Q_0 e^{-t/RC}$$

• Charging of a capacitor through a resistor Kirchoff's voltage law (loop rule):

$$V_0 - IR - \frac{Q_C}{C} = 0 \quad \longrightarrow \quad V_0 - RC \frac{dV_C}{dt} - V_C = 0,$$



Figure 4.2: Simple *RC* cicuit with explicitly drawn input and output.

or

$$(V_0 - V_C) + RC \frac{d}{dt}(V_0 - V_C) = 0,$$
  
$$\frac{d}{dt}(V_0 - V_C) = -\frac{1}{RC}(V_0 - V_C).$$

Initial Condition:

$$V_C(0) = 0.$$

Solution:

$$V_C(t) = V_0 \left( 1 - e^{-t/RC} \right)$$

and

$$V_R(t) = I(t)R = \frac{dQ_C}{dt}R = V_0 e^{-t/RC}.$$

• Characteristic time/decay time/time constant:  $\tau = RC$ .



Figure 4.3: Simple *RC* cicuits with implied input and output circuit elements. This circuit is known as an *integrator*.



Figure 4.4: Simple *RC* cicuits with implied input and output circuit elements. This circuit is known as a *differentiator*.