Topic 7

Diodes

7.1 *I-V* Curve

Actual I-V curve for a real diode obtained in lab:



I-V curve for an idealized silicon diode:



7.2 Rules for diodes based on simple idealized *I-V* curves

First, determine if diode is forward biased or reverse biased.

- For forward-biased silicon diodes:
 - $-\Delta V_{\text{diode}} \simeq 0.6 \,\text{V}.$ (For other materials the voltage drop will be different.)
 - I_{diode} determined by rest of circuit.
- For reverse-biased diodes:
 - $-I_{\text{diode}}\simeq 0.$
 - ΔV_{diode} determined by rest of circuit.

7.3 Diode circuits

- Diodes as rectifiers (as in lab).
- Diodes as voltage clamps.
- Diodes as protection with induitve loads.