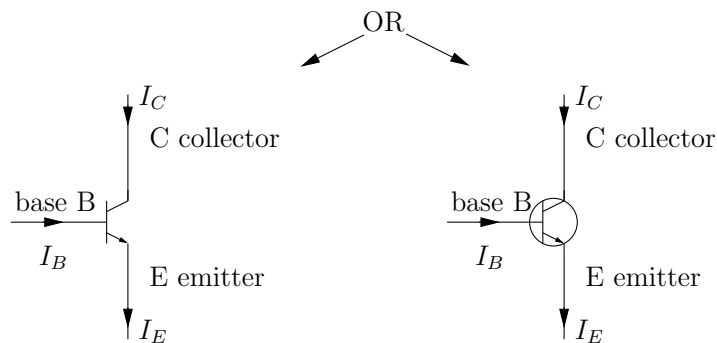


# Topic 8

## Transistors

We will only consider bipolar NPN transistors:



### 8.1 Models of transistor behavior

#### 8.1.1 The “simplest model” of transistor behavior

- $I_B \simeq 0$ .
- Current will flow in at the collector and out at the emitter (with  $I_C \simeq I_E$ ) if
  - the collector is more positive than the emitter, and
  - the base-emitter junction is forward biased (like a silicon diode).
- the magnitude of the collector-emitter current is determined by the rest of the circuit.

### 8.1.2 The “simple model” of transistor behavior

- Current will flow in at the collector and out at the emitter if
  - the collector is more positive than the emitter, and
  - the base-emitter junction is forward biased (like a silicon diode).
- The base current is small, but not zero. The magnitude of the base current is determined by the rest of the circuit along with base-emitter junction considered as a silicon diode ( $\Delta V_{BE} = 0.6 \text{ V}$ ).

When the rules above are obeyed, the relationship between the collector current and the base current is given by


$$I_C = \beta I_B,$$

where  $\beta$  is a number in the range of 75–100 for many common transistors. KCL still applies:


$$I_B + I_C = I_E \quad \longrightarrow \quad I_B(1 + \beta) = I_E.$$

## 8.2 Transistor Applications


### 8.2.1 Transistor as a switch

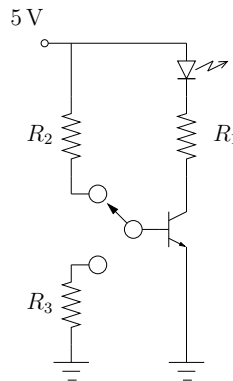

### 8.2.2 Constant current source

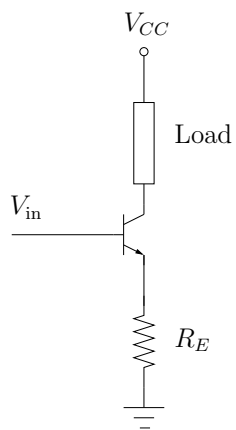

### 8.2.3 Emitter follower

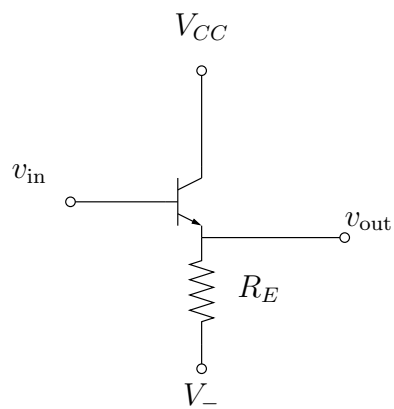

### 8.2.4 Common emitter amplifier

